

Truth Table

INPUT					OUTPUT			
A[0] (MSB)	A[1] (LSB)	B[0] (MSB)	B[1] (LSB)	Comparison	Color	Red	Green	Blue
0	0	0	0	A=B	Yellow	1	1	0
0	0	0	1	A<B	Cyan	0	1	1
0	0	1	0	A<B	Cyan	0	1	1
0	0	1	1	A<B	Cyan	0	1	1
0	1	0	0	A>B	Purple	1	0	1
0	1	0	1	A=B	Yellow	1	1	0
0	1	1	0	A<B	Cyan	0	1	1
0	1	1	1	A<B	Cyan	0	1	1
1	0	0	0	A>B	Purple	1	0	1
1	0	0	1	A>B	Purple	1	0	1
1	0	1	0	A=B	Yellow	1	1	0
1	0	1	1	A<B	Cyan	0	1	1
1	1	0	0	A>B	Purple	1	0	1
1	1	0	1	A>B	Purple	1	0	1
1	1	1	0	A>B	Purple	1	0	1
1	1	1	1	A=B	Yellow	1	1	0

K-MAPS and Inferred Circuit:

For RED color:

$\begin{matrix} b[0] & b[1] \\ a[0] & a[1] \end{matrix}$	00	01	11	10
00	1			
01	1	1		
11	1	1	1	1
10	1	1		1

$$\bar{b}[0]\bar{b}[1] + a[1]\bar{b}[0] + a[0]\bar{b}[0] + a[1]a[0] + a[0]b[0]\bar{b}[1]$$

For GREEN color:

$\begin{matrix} b[0] & b[1] \\ a[0] & a[1] \end{matrix}$	00	01	11	10
00	1	1	1	1
01		1	1	1
11			1	
10			1	1

$$\bar{a}[0]\bar{a}[1] + \bar{a}[0]b[1] + b[0]\bar{a}[0] + b[0]b[1] + b[0]a[0]\bar{a}[1]$$

For BLUE color:

$\begin{matrix} b[0] & b[1] \\ a[0] & a[1] \end{matrix}$	00	01	11	10
00		1	1	1
01	1		1	1
11	1	1		1
10	1	1	1	

$$\bar{b}[0]a[0] + b[0]\bar{a}[0] + \bar{b}[1]\bar{a}[0]a[1] + a[0]a[1]\bar{b}[1] + b[1]\bar{b}[0]\bar{a}[1] + b[0]b[1]\bar{a}[1]$$

Circuit diagram from K-Maps:


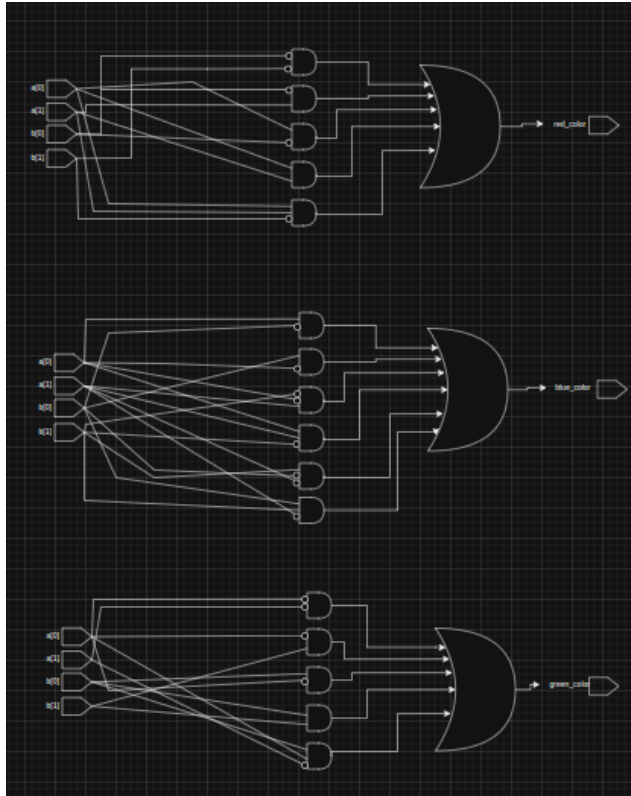


Diagram inferred by Xilinx Vivado:

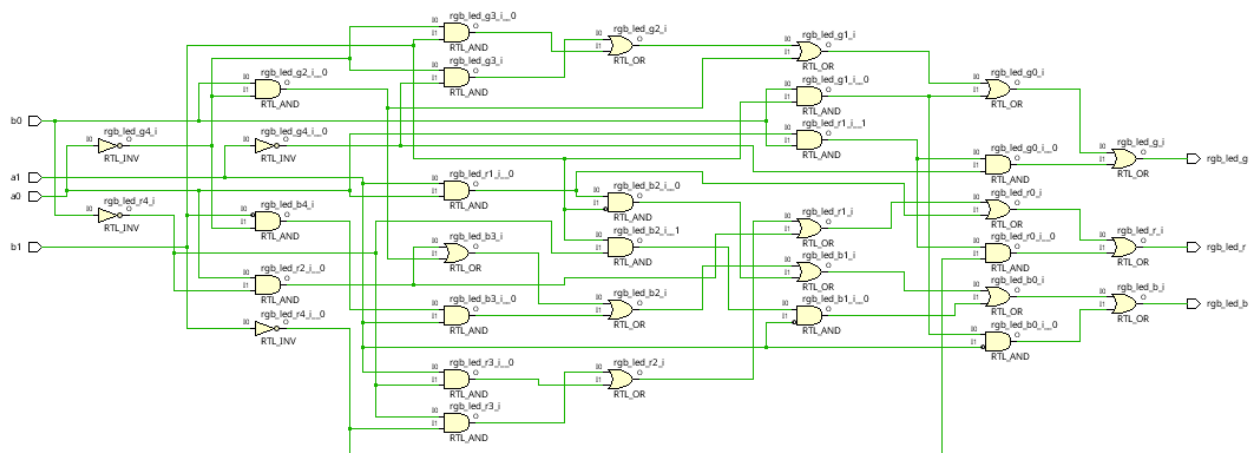

After testing of the SystemVerilog code in QuestaSim, and comparing it with the truth table above, the inferred circuit diagram is similar to the circuit diagrams from K-Maps.


Combinational Delay:

Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	3	2	3	a1	rgb_led_b	9.842	5.140	4.701	∞	input port cl
↳ Path 2	∞	3	2	3	a1	rgb_led_g	9.464	5.377	4.087	∞	input port cl
↳ Path 3	∞	3	2	3	a1	rgb_led_r	8.665	5.130	3.535	∞	input port cl
Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 4	∞	3	2	3	b1	rgb_led_r	2.203	1.504	0.699	-∞	input port cl
↳ Path 5	∞	3	2	3	b1	rgb_led_g	2.529	1.586	0.943	-∞	input port cl
↳ Path 6	∞	3	2	3	b1	rgb_led_b	2.770	1.514	1.256	-∞	input port cl

Maximum Combinational Delay is from a1 to rgb_led_b with 9.842s.

Resource Utilization:

Resource	Utilization	Available	Utilization %
LUT	2	63400	0.00
IO	7	210	3.33

 

2 out of 63400 LUTs and 7 out of 210 I/O were utilized.

SystemVerilog code of the circuit:

```
`timescale 1ns / 1ps

module rgb_module_code( input a0, input a1, input b0, input b1, output rgb_led_r, output
rgb_led_g, output rgb_led_b );

assign rgb_led_r = (b0 & ~b1) | (a1 & ~b0) | (a0 & ~b0) | (a1 & a0) | (a0 & b0 & ~b1);

assign rgb_led_g = (a0 & a1) | (a0 & b1) | (b0 & a0) | (b0 & b1) | (b0 & a0 & ~a1);

assign rgb_led_b = (b0 & a0) | (b0 & a0) | (b1 & ~a0 & a1) | (a0 & a1 & ~b1) | (b1 & ~b0 & ~a1) |
(b0 & b1 & ~a1);

endmodule
```